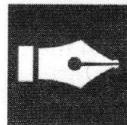


Name .....

Class.....

Roll No.....

Time  
25 Min.Max.  
MarksMarks  
Obtained  
17

## TOPIC-1

### Electric Current

**Q. 1.** State in brief the meaning of an electric circuit. [Board Term I, Set (34); 2010 (C2), 2011] (1)

Ans. ....

.....

**Q. 2.** State the relationship between 1 ampere and 1 coulomb. [Board Term I, Set (36), 2011] (1)

Ans. ....

.....

**Q. 3.** State the physical quantity which is equal to the ratio of potential difference and current. Define its SI unit. [Board Term I, Set (44), 2012] (2)

Ans. ....

.....

.....

.....

.....

.....

**Q. 4.** List in a tabular form two differences between a voltmeter and an ammeter.

[Board Term I, Set (43), 2012] (2)

Ans. ....

.....

.....

.....

.....

.....

**Q. 5.** Name and define S.I. unit of resistance. Calculate the resistance of a resistor if the current flowing through it is 200 mA, when the applied potential difference is 0.8 V.

[Board Term I, Set (41), 2012] (3)

Ans. ....



.....

**Q. 6.** Define resistance. Write the SI unit of resistance. Match the correct range of resistivity with the materials given :

- |                  |                                     |
|------------------|-------------------------------------|
| (i) Conductors   | (a) $10^{-6} \Omega m$              |
| (ii) Alloys      | (b) $10^{12}$ to $10^{17} \Omega m$ |
| (iii) Insulators | (c) $10^{-6}$ to $10^{-8} \Omega m$ |
- [Board Term I, Set (40), 2012] (3)

**Ans.** .....

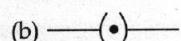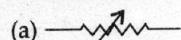**Q. 7.** (i) Name an instrument that measures electric current in a circuit. Define unit of electric current.  
(ii) What are the following symbols mean in an electric circuit.



- (iii) Draw a closed circuit diagram consisting of 0.5 m long nichrome wire XY, an ammeter, a voltmeter, four cells of 1.5 V and a plug key. [Board Term I, Set-OQKPLGV, 2016] (5)

**Ans.** .....

